

Lab Task 1:

Implement the FSM on FPGA

VHDL Code:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity FSMdiv is
    port (
        clk      : in std_logic;
        letstart  : in std_logic;
        remaind   : out std_logic_vector(3 downto 0);
        quot      : out std_logic_vector(3 downto 0)
    );
end FSMdiv;

architecture behav of FSMdiv is
    signal x : std_logic_vector(3 downto 0) := "1000"; -- 8
    signal y : std_logic_vector(3 downto 0) := "0011"; -- 3
    signal q : std_logic_vector(3 downto 0) := "0000"; -- For Quotient

    --define state using one hot coding
    constant initial : std_logic_vector(2 downto 0) := "001";
    constant compute : std_logic_vector(2 downto 0) := "010";
    constant done    : std_logic_vector(2 downto 0) := "100";

    -- State Memory
    signal mystate : std_logic_vector(2 downto 0) := initial;
begin
    process (clk)
    begin
        if (clk'event and clk = '1') then
            case mystate is
                -----
                when initial =>
                    -- Initialization of signals
                    x <= "1000"; -- 8
                    y <= "0011"; -- 3
                    q <= "0000"; -- Reset quotient

                    if (letstart = '1') then
                        mystate <= compute;
                    else
                        mystate <= initial;
                    end if;
                -----
                when compute =>
                    -- Perform subtraction and increment quotient
                    if (x >= y) then
                        x <= x - y;
                        q <= q + 1;
                    end if;

                    -- Check if we can continue subtracting
                    if (x >= y) then
```


```

        mystate <= compute;
    else
        mystate <= done;
    end if;
    -----
when done =>
    -- Output remainder and quotient
    remaind <= x;
    quot <= q;

    -- Go back to initial state
    mystate <= initial;
    -----
when others =>
    mystate <= initial;
    -----
end case;
end if;
end process;
end behav;

```

Simulation:

 

Simulation 1: Compute quotient and remainder after enabling positive edge trigger. The output is generated in 3 cycles.

Lab Task 2:

Implement a 4-bit sequence detector(1011)

VHDL Code:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity FSM_sequence_detactor is
    port (
        clk      : in std_logic;
        letstart : in std_logic;
        y        : out std_logic
    );
end FSM_sequence_detactor;

architecture bhv of FSM_sequence_detactor is

    --define state using one hot coding
    constant state0 : std_logic_vector(4 downto 0) := "00001";
    constant state1 : std_logic_vector(4 downto 0) := "00010";
    constant state2 : std_logic_vector(4 downto 0) := "00100";
    constant state3 : std_logic_vector(4 downto 0) := "01000";
    constant state4 : std_logic_vector(4 downto 0) := "10000";

    -- State Memory
    signal mystate : std_logic_vector(4 downto 0) := state0; -- 00001


begin
    process (clk)
    begin
        if (clk'event and clk = '1') then -- positive edge sensitive
            case mystate is
                -----
                when state0 =>
                    y <= '0';
                    if (letstart = '1') then
                        mystate <= state1;
                    else -- 0
                        mystate <= state0;
                    end if;
                -----
                when state1 =>
                    y <= '0';
                    if (letstart = '0') then
                        mystate <= state2;
                    else -- 1
                        mystate <= state1;
                    end if;
                -----
                when state2 =>
                    y <= '0';
                    if (letstart = '1') then
                        mystate <= state3;
                    else --0
                        mystate <= state0;
                    end if;
                -----
            end case;
        end if;
    end process;
end;
```

```

        end if;
    -----
    when state3 =>
        y <= '1';
        if (letstart = '1') then
            mystate <= state4;
        else -- 0
            mystate <= state2;
        end if;
    -----
    when state4 =>
        y <= '1';
        if (letstart = '1') then
            mystate <= state0;
        else -- 0
            mystate <= state0;
        end if;
    -----
    when others =>
        mystate <= state0;
    -----
end case;
end if;
end process;
end bhv;

```

Simulation:

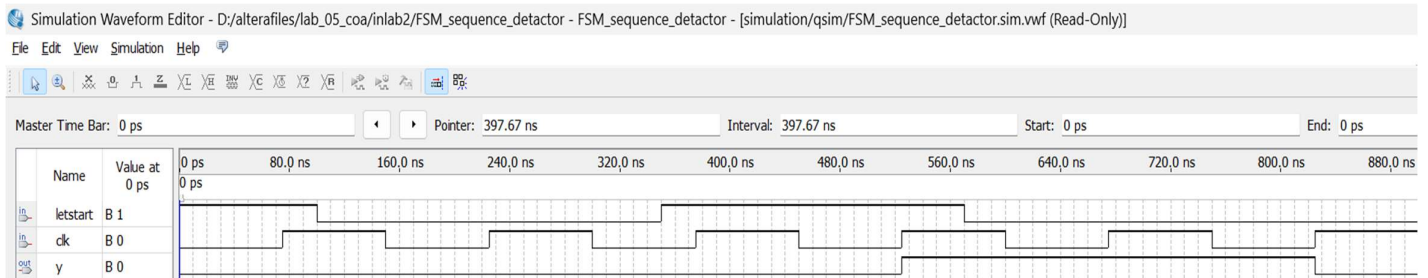

Simulation 2: detects the input(let start) pattern of 1011